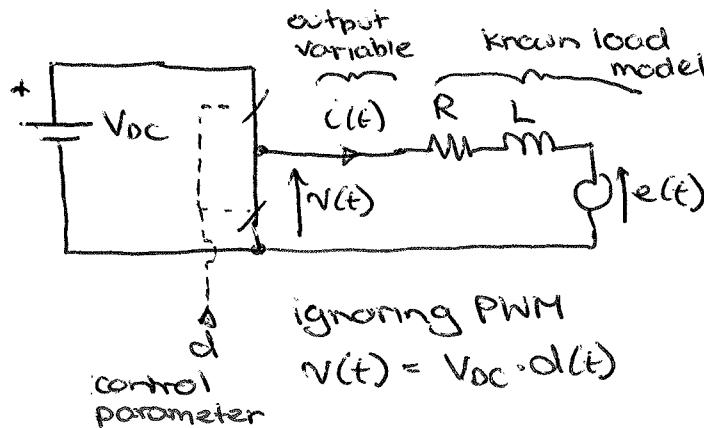


CURRENT REGULATORS FOR VOLTAGE-SOURCE INVERTERS

12R001

1. VOLTAGE-SOURCE INVERTER


with generic RLV load



can use duty-cycle to command a desired output voltage $V^*(t)$


$$\text{where } 0 \leq V^* \leq V_{dc}$$

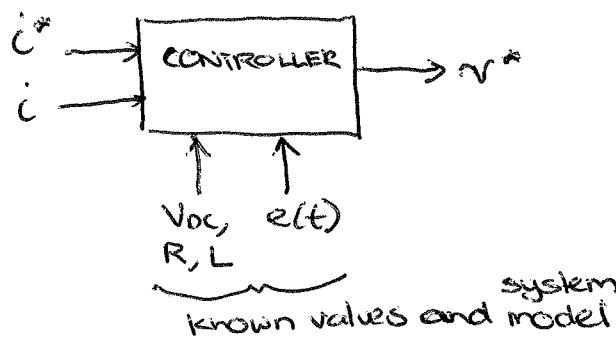desire to get i to track a reference command i^* by controlling V^*



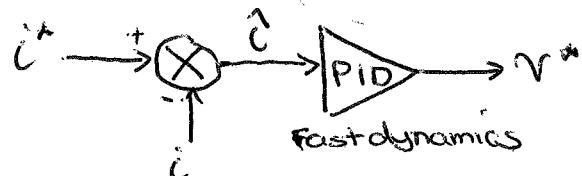2. FEEDBACK CONTROL

controls output based on difference between actual and command, does not use load model




$$V^* = K_d \cdot \frac{d}{dt}(i^* - i) + K_p(i^* - i) + K_i \cdot \int (i^* - i) dt$$

zero steady-state error for DC inputs


extreme case is

hysteresis controller

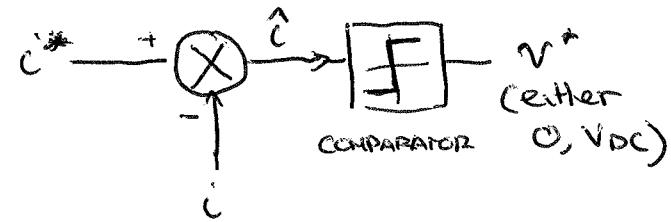

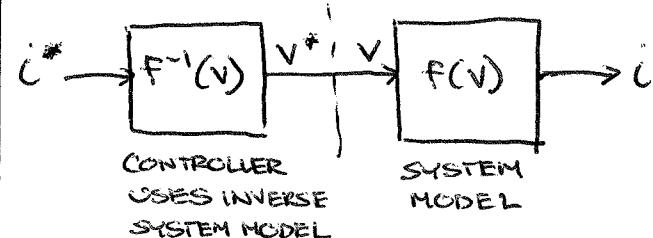3. FEEDFORWARD CONTROL

controls output based on reference command and system model, does not use actual output value (open-loop control)




For RLV load, can show

$$V^* = L \cdot \frac{di^*}{dt} + i^* R + e$$

DC current command \rightarrow DC voltage command
AC current command \rightarrow AC voltage command

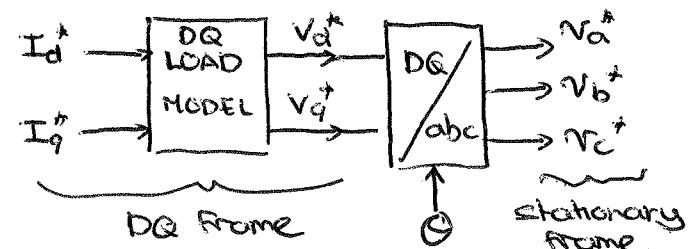can use d, q current commands for 3ph machines




Feedforward offers good transient performance but prone to steady-state errors due to model errors

CURRENT REGULATORS (CONT'D)

4. FEED BACK / FEED FORWARD

combine methods together

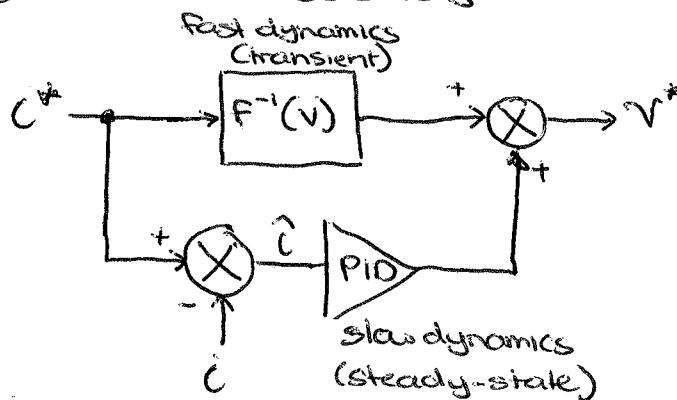

5. STATE BASED CONTROL

state variables define system state
(for RLV load $i = \text{state variable}$)

a model based control method which attempts to move system to desired final state

$$\begin{array}{ccc} \text{present state} & & \text{desired future state} \\ i_k & \longrightarrow & i_{k+1}^* \end{array}$$

choose

$$V_k^* = L \cdot \frac{\dot{i}_{k+1}^* - i_k}{\Delta t} + i_{k+1}^* R + e_{k+1}$$

particularly useful for controlling systems which are complex and have multiple inputs and outputs and strong interactions between inputs

simple example, three-phase inverter has three current output variables, but only two are independent